

Code : 041504

B.Tech 5th Semester Exam., 2015

ANALOG ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven of the following : $2 \times 7 = 14$

- (a) Explain the role of amplifiers. Write the name of five types of amplifier.
- (b) Explain the importance of gain bandwidth product.
- (c) Demonstrate the h -parameter.
- (d) Illustrate the difference between β_p and β_n .
- (e) Draw the circuit for Darlington pair.
- (f) Illustrate the -3dB cut-off frequency.
- (g) Define the difference between oscillator and amplifier.

- (h) Demonstrate the use of Wien bridge oscillator.
- (i) Determine the input impedance of OPAMP.
- (j) Explain noise figure and signal-to-noise ratio.

2. (a) Derive the expression for collector current. Define the CB, CE and CC configurations. Establish the relation between α , β and γ . 7
- (b) Define ideal voltage amplifier, current amplifier and ideal transconductance amplifier. 7
3. (a) Explain Darlington pair in detail with suitable circuit diagram and mathematical expressions. 7
- (b) Define the low-pass and high-pass filter, and calculate its cut-off frequencies and magnitude. 7
4. (a) Demonstrate the equivalent circuit for an emitter follower stage at high frequencies. 7
- (b) A three-stage system voltage gain is 180 dB. The second-stage has twice of first-stage and third has 0.3 times of first. Calculate the voltage gain of the system in each stage. 7

5. (a) Design the Wien bridge oscillator and derive the mathematical expression for calculation of the frequencies. 7
- (b) Explain the transmission path loss. Derive the Friis transmission formula and define all the terms. 7
6. (a) Define Hartley and Colpitts oscillator. Design T- and star-network, and calculate the input and output impedance. 7
- (b) In Colpitts oscillator the value of C_1 and C_2 are in the ratio of $20 \mu\text{F}/2 \mu\text{F}$. Calculate the value of inductance for oscillation frequency 100 kHz. 7
7. (a) Explain the noise. Explain the difference between thermal noise and flicker noise. 7
- (b) Define tuned amplifier with suitable diagram. 7
8. (a) Demonstrate class AB amplifier in detail with suitable mathematical expression and diagram. 7
- (b) A transformer-coupled class A amplifier drives a load of 18Ω through 4 : 1 transformer. With $V_{CC} = 25 \text{ V}$, the circuit derives 3 watt to the load. The transformer efficiency is 85%. Find power loss of the primary transformer and r.m.s. value of load current. 7

9. Write short notes on any two of the following : 7×2=14
- (a) High-frequency amplifier
- (b) Flicker noise
- (c) R-C phase shift oscillator
