

7. (a) What are the different types of compensation that can be achieved in smart sensors? 7
- (b) Explain in brief the protocol for communication between host and smart sensor. 7
8. (a) Explain briefly the following terms with respect to an ADC : 2×4=8
- (i) Quantization error
  - (ii) Resolution
  - (iii) Aperture time
  - (iv) Coding
- (b) An analog voltage signal whose highest significant frequency is 1KHz is to be digitally coded with a resolution of 0.01% covering a voltage range of 0-10 V :
- (i) Determine minimum number of bits in the digital code.
  - (ii) Determine r.m.s. value of quantization error.
  - (iii) Determine aperture time. 6
9. Write short notes on the following : 7×2=14
- (a) Phase-locked loop
  - (b) R-2R digital to analog converter

\*\*\*

Code : 041606

B.Tech 6th Semester Exam., 2015

INTELLIGENT INSTRUMENTATION

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven of the following questions : 2×7=14

~~(a)~~ A differential amplifier having CMRR 50,000 has a difference mode gain of 500. Calculate its common mode gain.

~~(b)~~ An active half-wave voltage follower circuit has an input of  $10 \sin \omega t$  V. If the input resistance is 2 kΩ and feedback resistance is 10 kΩ, find the expression for the output voltage.

~~(c)~~ List the desirable properties of an ideal OPAMP.

(d) Give the expression for the gain of a high-pass filter at a frequency  $\omega$ , if its time constant is  $\tau$ .

(f) State the condition when a low-pass RC filter acts as pure integrator.

(g) An 8-bit converter is used for a d.c. range of 0-10 V. Find the weight of LSB.

(g) A successive approximation ADC has a resolution of 20 mV. What will be its digital output for an analog input of 2.17 V?

(h) The 0-10 V ADC has to have a resolution of 0.025%. Find the r.m.s. value of quantization error.

(i) Define accuracy.

(j) How many different voltages can be output for a DAC with 6-bit resolution?

2. (a) Discuss the different features that differentiate an 'intelligent instrumentation' system from a 'dumb instrumentation system'. 7

(b) Discuss the components of an intelligent instrumentation system with the help of a block diagram. 7

(c) Draw the circuit diagram of an instrumentation amplifier and derive the expression for gain. 7

(b) Derive the expression for transfer function of a band-pass RC filter. Draw its characteristics and also the Bode diagram. 7

4. (a) What are active filters? Describe a low-pass active filter and derive the expression for its cut-off frequency. Also, draw its frequency characteristics. 7

(b) Design a high-pass filter with a characteristic resistance of 50Ω and a cut-off frequency of 20 MHz and an attenuation of 80 dB at 5 MHz. 7

5. (a) Explain the working of current to voltage converter with a circuit diagram. Compare it with a voltage follower circuit. 8

(b) Briefly explain the working of the following : 3×2=6  
(i) Signal Integrator  
(ii) Signal Multiplier

6. (a) Discuss smart sensor with the help of a block diagram.

(b) What do you mean by primary smart sensor? What are the application areas of smart sensor? 7