

WEEKLY TEST EXAM – WEEK 1st

5th SEMESTER ELECTRONICS AND COMMUNICATION

ANALOG ELECTRONICS

FULL MARKS-20

TIME-20 MINUTES

- *Attempt all questions, each question carries 2 marks.*
 - *There is no negative marking.*
-

1. Early effect or Base width modulation occurs in which of the following semiconductor devices?

- a) BJT b) MOSFET c) PN diode d) Zener diode

2. In BJT current is mainly due to .

- a) Diffusion of carriers b) Drift of the carriers c) Both (a) and (b) d) None of these

3. A region of –ve differential resistance is observed in the current voltage characteristics of silicon P-N junction if

- a) Both the P-region and N-region are heavily doped.
b) N-region is heavily doped compared to P-region.
c) P-region is heavily doped compared to N-region.
d) Intrinsic silicon is inserted between P- and N- region.

4. If for a silicon N-P-N transistor, the base – to – emitter voltage is 0.7V and the collector – to – base voltage is 0.2V, then the transistor is operating in the

- a) Active region b) Saturation region c) Reverse active region d) cut-off region

5. Consider the following statements S1 and S2

S1 : The β of a bipolar transistor reduces if the base width is increased.

S2 : The β of a bipolar transistor increases if the doping concentration in the base is increased


Which of the following is correct?

- a) S1 is false and S2 is true. b) Both S1 and S2 are true.
c) Both S1 and S2 are false. d) S1 is true and S2 is false.

6. A silicon PN junction at a temperature of 20⁰ C has a reverse saturation current of 10 pico amperes(pA). The reverse saturation current at 40⁰ C for the same bias is approximately


- a) 30pA b) 40pA c) 50pA d)60pA

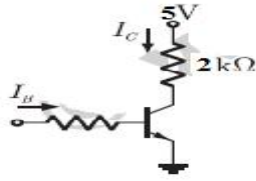7. Assuming $V_{CEsat} = 0.1$ V and $\beta = 100$, the minimum base current (I_B) required to drive the transistor in the figure to saturation is




- a) $24 \mu\text{A}$ b) $24.5 \mu\text{A}$ c) $49 \mu\text{A}$ d) 2.45mA

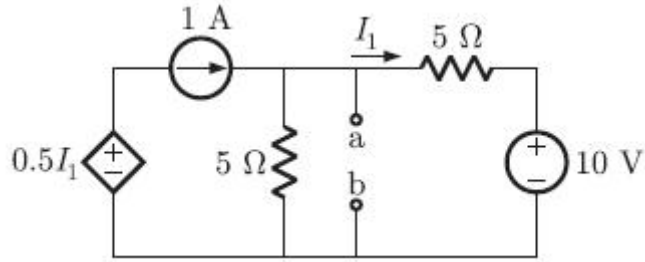8. For the circuit shown in the figure, Thevenin's voltage at terminals a - b is




- a) 5V b) 7.5V c) 4V d) 3V

9. The Voltage V_0 in the figure is

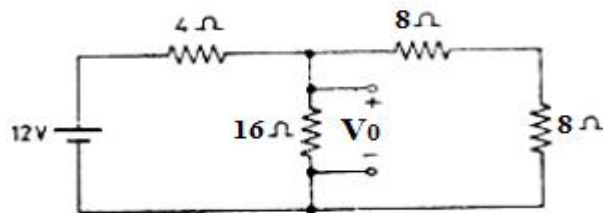

- a) 4V b) 16V c) 12V d) 8V

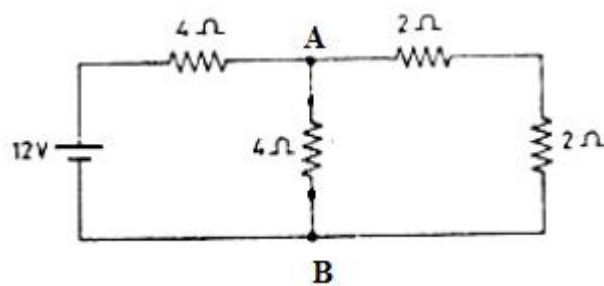10. In the given network find thevenin resistance across terminal A-B



- a) 4 b) $4/3$ c) 2 d) 8