

WEEKLY TEST EXAM – WEEK 2nd 23-07-18

5th SEMESTER ELECTRONICS AND COMMUNICATION

ANALOG ELECTRONICS

FULL MARKS-20

TIME-30 MINUTES

1. A Silicon diode is biased at 1mA current and working at 327° C temperature, value of small signal diode resistance ----- . (Given, $V_T = 25\text{mV}$ at 27° C.)

2. Consider the following statements S1 and S2

S1: The β of a bipolar transistor increases if the base width is increased.

S2: The β of a bipolar transistor increases if the doping concentration in the base is increased

Which of the following is correct?


- a) S1 is false and S2 is true.
- b) Both S1 and S2 are true.
- c) Both S1 and S2 are false.
- d) S1 is true and S2 is false.

3. The magnitude of gain of fixed biased CE amplifier is 25, if a sinusoidal signal of 20 mV peak amplitude is applied to this amplifier. What will be the magnitude of output signal?

- a) - 0.5V
- b) 12.5mV
- c) 20mV
- d) 0.5V


4. What is the region of operation for the transistor shown? [$\beta = 100$, $V_{BE,active} = 0.7\text{V}$, $V_{BE,saturation} = 0.8\text{V}$, $V_{CE,saturation} = 0.2\text{V}$]

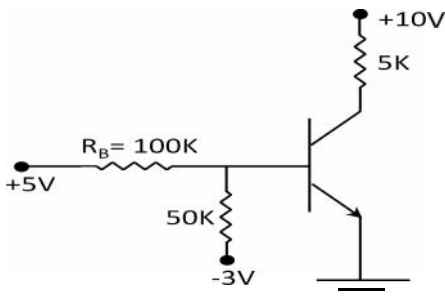- (a) Active
- (b) Saturation
- (c) Reverse Active
- (d) cut-off




5. Consider CE amplifier given below: $\beta = 75$

The mid-band voltage gain $\left| \frac{V_o}{V_i} \right|$ is: -----

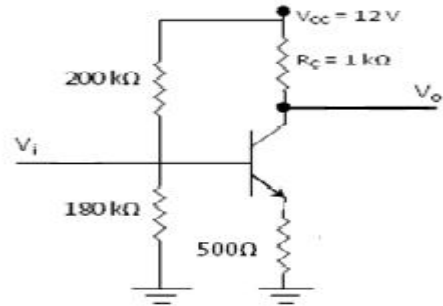


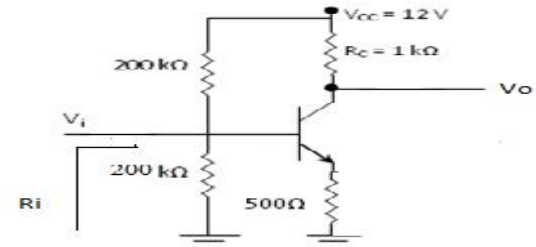6. The input impedance, R_i for the CE amplifier shown in the figure below is: Use $V_T = 26\text{ mV}$, $\beta = 80$, $r_o \rightarrow \infty$



- (a) 0.69 k
- (b) 29 k
- (c) 41 kΩ
- (d) 100 k

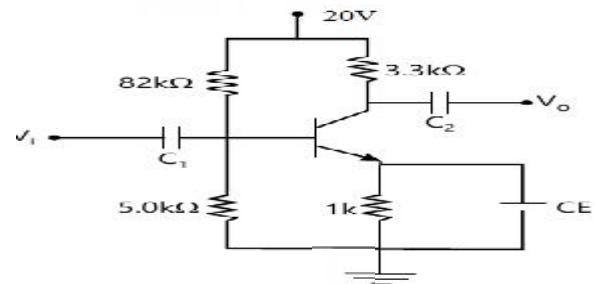7. Determine the transconductance (g_m), output resistance(r_o) and r_{π} for the circuit given below,



Where, early voltage (V_A) = 100V and $\beta = 100$

8. Draw the small signal model for circuit given below:

