


SOLUTION OF MID-SEM EXAM PAPER (NOV 2018)

SEM-V; BRANCH-EE; PAPER: ANALOG ELECTRONICS.

(i) (d) Using current-shunt f/b means the sample is taken from o/p current and ^{at} the i/p, it is connected in shunt ~~with~~ through f/b n/w to the i/p current. Hence, such a feedback topology is used in a current amplifier which ideally has a zero i/p imp. and infinite o/p imp.

Hence, the feedback (since it tends the performance to the ideal one) will decrease i/p imp and increase o/p imp.

(ii) (b)

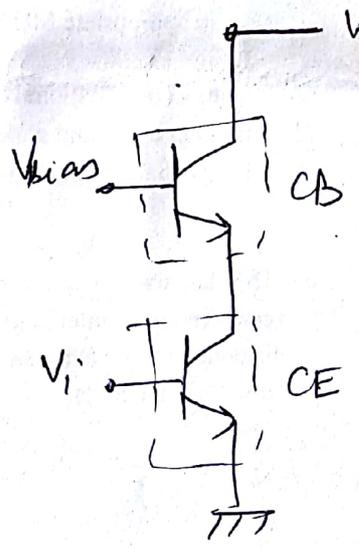


A cascode amp is a CE-CB configuration

~~(scribble)~~

P.T.O.

(iii) (c)

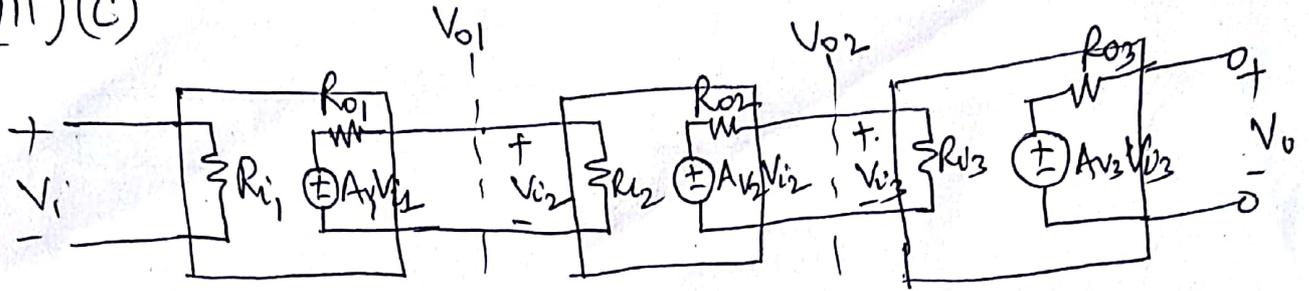

$R_{i1} = R_{i2} = R_{i3} = 1\text{ k}\Omega$
 $A_{v1} = A_{v2} = A_{v3} = 50$
 $R_{o1} = R_{o2} = R_{o3} = 250\ \Omega = 0.25\text{ k}\Omega$

$$A_v = \frac{V_o}{V_i} = \frac{V_o}{V_{o2}} \times \frac{V_{o2}}{V_{o1}} + \frac{V_{o1}}{V_i}$$

$V_{o2} = V_{i3}$ & $V_{o1} = V_{i2}$ & $V_{i1} = V_i$

$$\Rightarrow A_v = \frac{V_o}{V_{i3}} \times \frac{V_{o2}}{V_{i2}} \times \frac{V_{o1}}{V_{i1}} \quad \text{--- (1)}$$

$$\Rightarrow A_v = \left(\frac{A_{v3} V_{o3}}{V_{i3}} \right) \times \left(\frac{A_{v2} V_{o2} \times R_{i3}}{(R_{o2} + R_{i3}) V_{i2}} \right) \times \left(\frac{A_{v1} V_{o1} \times R_{i2}}{(R_{o1} + R_{i2}) V_i} \right)$$

$$= A_{v3} \cdot A_{v2} \cdot A_{v1} \cdot \frac{R_{i3}}{(R_{o2} + R_{i3})} \cdot \frac{R_{i2}}{(R_{o1} + R_{i2})}$$


$$= 50 \times 50 \times 50 \times \frac{1}{1.25} \times \frac{1}{1.25}$$

$$= 80,000$$

in dB; $20 \log_{10} A_v \approx 98\text{ dB}$ Ans

(IV) (b)

For a CE amplifier:

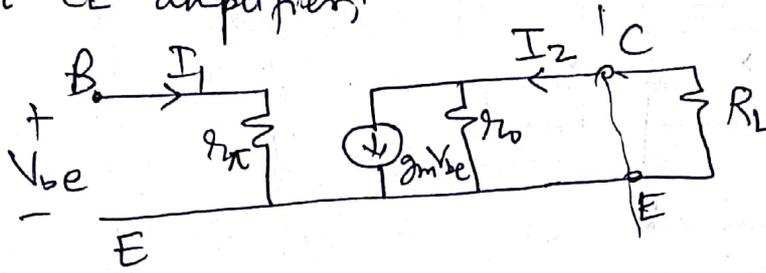

Current gain; $A_I = -\frac{I_2}{I_1}$

$$I_1 = \frac{V_{be}}{r_\pi}$$

$$\& -I_2 = -g_m V_{be} \cdot \frac{r_o}{r_o + R_L}$$

$$\Rightarrow A_I = \left(-\frac{g_m V_{be} \cdot r_o}{r_o + R_L} \right) \left(\frac{1}{V_{be}/g_m} \right)$$

$$= -\frac{g_m r_o r_\pi}{r_o + R_L}$$

if $r_o \gg R_L$,

$$A_I \approx -g_m r_\pi$$

$$\Rightarrow |A_I| = g_m r_\pi \quad \underline{A_{ms}}$$

(V) (b)


This is a Colpitt oscillator with $f_{osc} = \frac{1}{2\pi \sqrt{L C_{eq}}}$

where $C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{2 \times 2}{2 + 2} = 1 \text{ pF}$

$$\Rightarrow f_{osc} = \frac{1}{2\pi \sqrt{10 \times 10^{-6} \times 10^{-12}}} = \frac{1}{2\pi \times 3.16 \times 10^{-9}}$$

$$= 50.39 \text{ MHz}$$

(2)

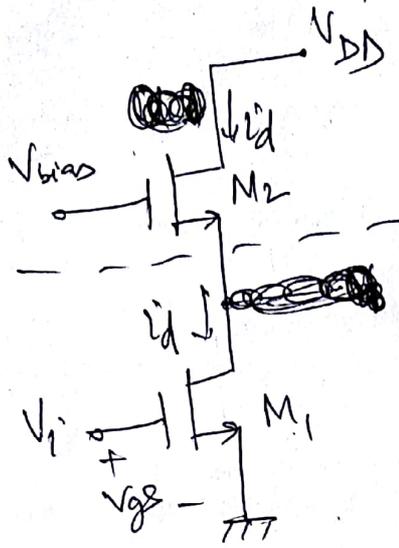


$$i_{d1} = i_{d2} = i_d$$

$$R_{o2} = \frac{r_{o2}}{1 + g_{m2} r_{o2}}$$

M₂ acts as a load for M₁ with $R_{o2} = \frac{r_{o2}}{1 + g_{m2} r_{o2}}$

Considering small signal model:

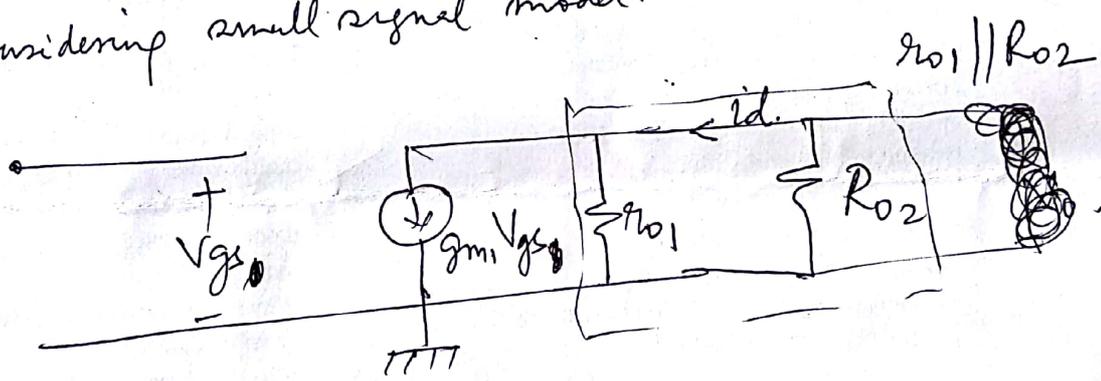

(i) Calculation of overall gm: $(g_m = \frac{\partial i_d}{\partial V_{gs}})$

$$\text{Now, } i_d = \frac{g_{m1} V_{gs1} \cdot r_{o1}}{R_{o2} + r_{o1}}$$

$$\Rightarrow \frac{\partial i_d}{\partial V_{gs}} = g_m = \frac{g_{m1} r_{o1}}{r_{o1} + R_{o2}} = \frac{g_{m1} r_{o1}}{r_{o1} + \frac{r_{o2}}{1 + g_{m2} r_{o2}}}$$

if $g_{m2} r_{o2} \gg 1$, then

$$g_m \approx \frac{g_{m1} r_{o1}}{r_{o1} + 1/g_{m2}}$$

Ans.

P.T.O.

NOTE: This expression can be further simplified as follows:


$$g_m \approx \frac{g_{m1} r_{o1} \cdot g_{m2}}{r_{o1} g_{m2} + 1}$$

If $g_{m2} r_{o1} \gg 1$


$$\Rightarrow g_m \approx \frac{g_{m1} r_{o1} \cdot g_{m2}}{r_{o1} g_{m2}}$$

$$\Rightarrow g_m \approx g_{m1} \underline{\underline{A_{v0}}}$$

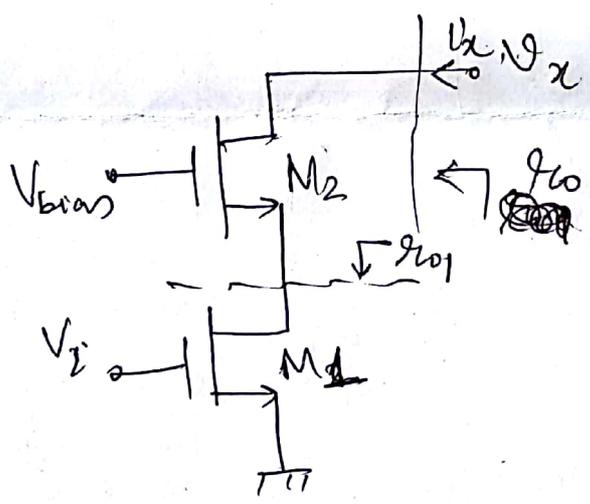(ii) Calculation of $r_{o} = \frac{\partial V_{ds}}{\partial i_d} = \frac{V_x}{i_x}$



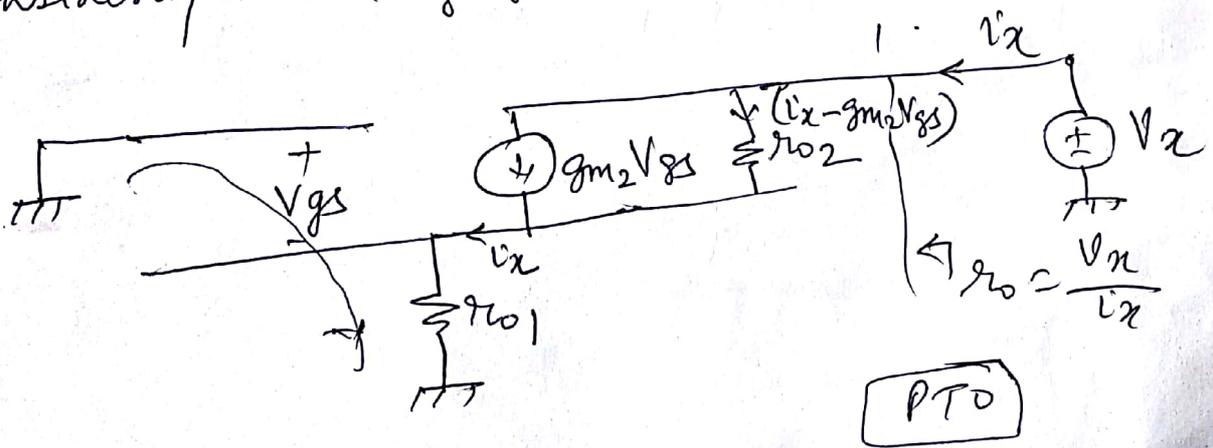For calculation of r_o ; V_P voltage source must be short-circuited. M_1 will appear as ~~a load~~ r_{o1} for M_2 .
Considering small signal model.



P.T.O

Now, applying KVL in i/p loop:

$$V_{gs} + i_x r_{o1} = 0 \Rightarrow V_{gs} = -i_x r_{o1} \quad \text{--- (1)}$$

Applying KVL in o/p loop:

$$V_x = (i_x - g_{m2} V_{gs}) r_{o2} + i_x r_{o1}$$

$$= (i_x + i_x g_{m2} r_{o1}) r_{o2} + i_x r_{o1}$$


$$\Rightarrow \frac{V_x}{i_x} = (1 + g_{m2} r_{o1}) r_{o2} + r_{o1}$$

$$\Rightarrow \boxed{r_o = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2}} \text{ Ans.}$$

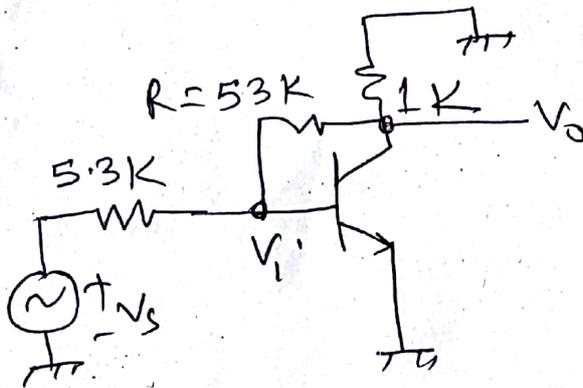(3) Since $h_{ie} = \infty \Rightarrow I_b = 0$

but since $h_{fe} \rightarrow \infty \Rightarrow I_c$ is finite

For small signal analysis, let us redraw the ckt as follows:




Using Miller's theorem:

$$R_1 = \frac{R}{1-K} \text{ and } R_2 = \frac{R}{1-K} \approx R = 53K$$

where ~~$K = A_v = \left(\frac{V_o}{V_i} \right)$~~ $K = \frac{V_o}{V_i}$

[PTO]

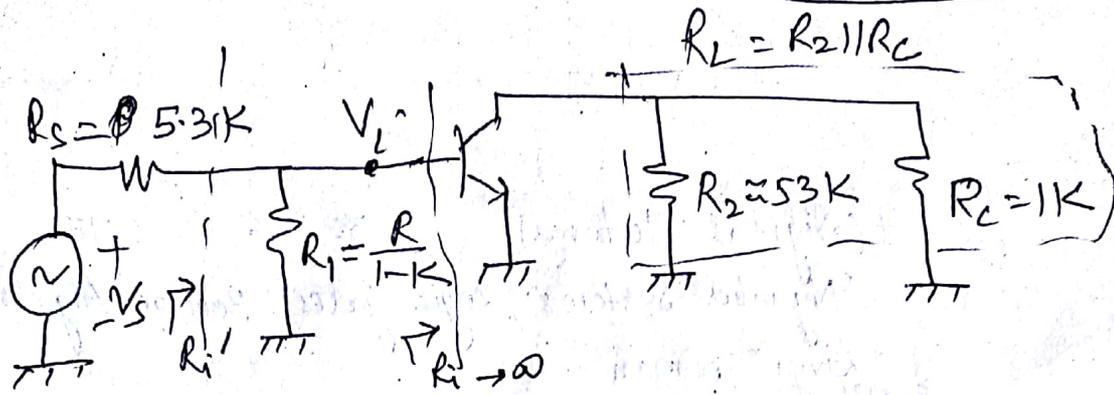

$$R_L = R_2 \parallel R_C = 53 \parallel 1 = 0.981 \text{ k}\Omega.$$

$$\text{Voltage gain, } K = \frac{V_o}{V_i} = -\frac{h_{fe} R_L}{R_i} \approx -R_L = -981$$

$$[\because h_{fe} \rightarrow \infty \text{ and } R_i = h_{ie} \rightarrow \infty]$$

$$\Rightarrow R_1 = \frac{R}{1-K} = \frac{53}{1+981} = 54 \Omega$$

$$V_i = \frac{R_1}{R_s + R_1} V_s = \frac{54}{54 + 5300} V_s$$


$$\Rightarrow \frac{V_i}{V_s} \approx 0.01$$

$$\Rightarrow \text{Voltage gain, } A_{Vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = K \frac{V_i}{V_s}$$

$$\text{or, } A_{Vs} = -981 \times 0.01$$

$$\text{or, } \boxed{A_{Vs} = -9.81 \text{ Ans.}}$$

4(i)

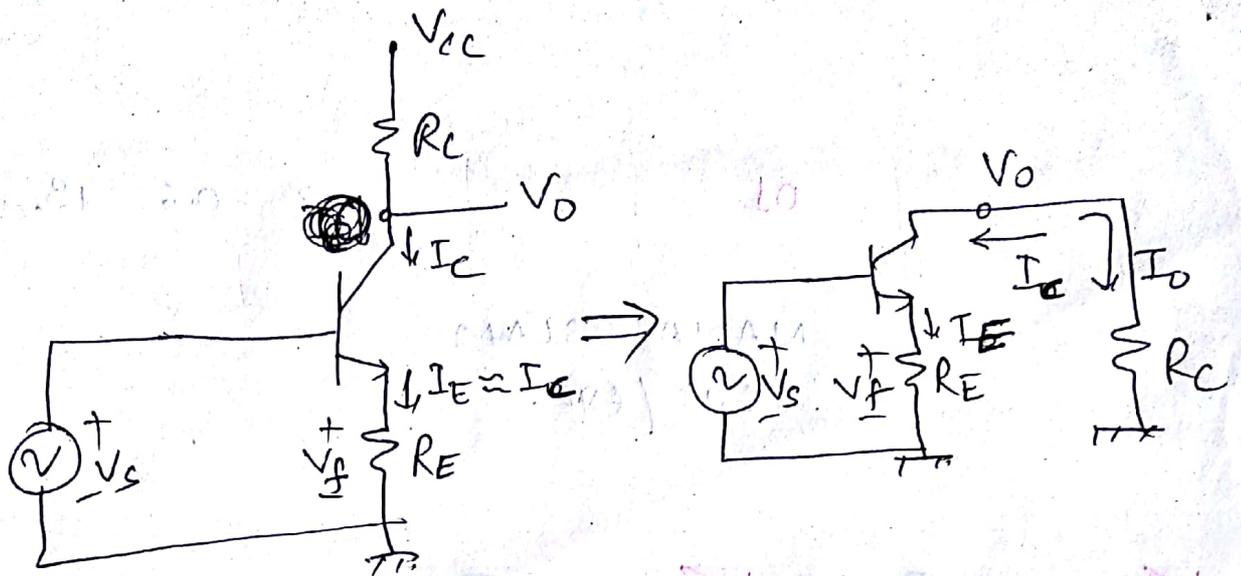


feedback topology: Current-series
 The sampled signal is the load current \$I_0\$ and the feedback signal is voltage \$V_f\$ across \$R_E\$.

$$\beta = \frac{V_f}{I_0} = \frac{I_E R_E}{I_0}$$


but $I_E \approx I_C = -I_0$
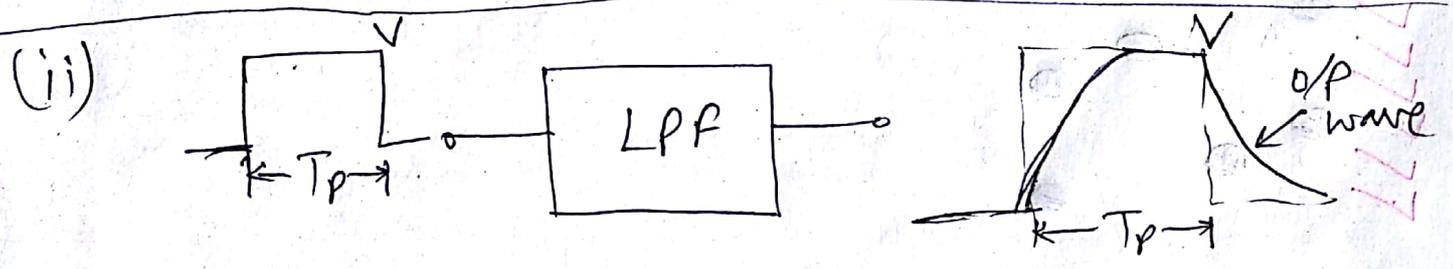
$$\Rightarrow \beta = -\frac{I_0 R_E}{I_0} = -R_E \quad \text{Ans.}$$



Let us consider a simple RC n/w as a first order LPF.

PTO

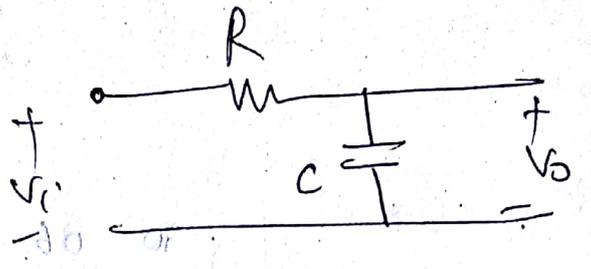

Since the capacitor voltage cannot change instantaneously, the o/p starts from zero and rises towards the steady state value 'V'.

The o/p is given as:

$$V_o = V(1 - e^{-t/RC}) \quad \text{--- (1)}$$

where RC is the charging time constant, 'T'.
 Now 'T' also decides the high 3dB freq. of the amplifier used to amplify this signal without excessive distortion.

Let us consider rise time, t_r be the time required for 10% rise in o/p voltage. Then from eqn (1),

$$\Rightarrow 0.1V = V(1 - e^{-t_r/RC})$$

$$\Rightarrow t_r = 2.2RC = \frac{0.2}{2\pi f_H} = \frac{0.35}{f_H}$$

where $2\pi f_H = \frac{1}{T}$ or; $f_H = \frac{1}{2\pi RC}$

Choosing f_H equal to the reciprocal of pulse width,

$(f_H = \frac{1}{T_p})$; we have $t_r = 0.35 T_p$

Q.5(i)&(ii) are Q.6 are derivations or theoretical questions which are present in class notes.