


Intelligent Instrumentation

Q.2. All-Pass filter - OP-AMP:-

$$\frac{V_p - U_{in}}{R} + \frac{U_p}{(1/sC)} = 0$$

$$U_p \left[\frac{1}{R} + sC \right] = \frac{U_{in}}{R}$$
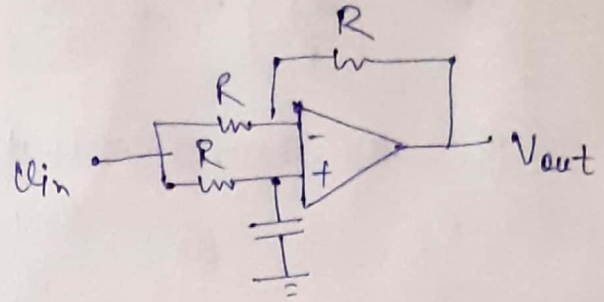
$$V_p \left[\frac{1 + R s C}{R} \right] = \frac{U_{in}}{R} \Rightarrow U_p = \frac{U_{in}}{(1 + R s C)} \quad \text{--- (1)}$$



$$\frac{U_p - U_{in}}{R} + \frac{U_p - U_o}{R} = 0$$

$$2U_p = U_o + U_{in} \Rightarrow \frac{2U_{in}}{1 + R s C} - U_{in} = U_o$$

$$U_{in} \left[\frac{2 - (1 + R s C)}{1 + R s C} \right] = U_o$$

$$U_{in} \left[\frac{1 - R s C}{1 + R s C} \right] = U_o \Rightarrow \frac{U_o}{U_{in}} = \frac{(1 - R s C)}{(1 + R s C)}$$


$$\left| \frac{U_o}{U_{in}} \right| = \left| \frac{\sqrt{1 + (sC)^2}}{\sqrt{1 + (sC)^2}} \right| = 1$$

Pole

Phase: $-\tan^{-1}(\omega R C) - \tan^{-1}(\omega R C)$

$= -2 \tan^{-1}(\omega R C)$ at $\omega = 1/R C$

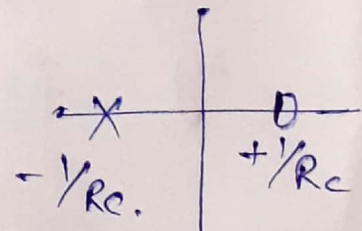$-2 \tan^{-1}\left(\frac{R C}{R C}\right) = -90^\circ$



Q.4

The output V_o for summing amplifier:-

$$V_o = \left[\left(\frac{R_f}{R_1} \right) V_1 + \left(\frac{R_f}{R_2} \right) V_2 + \left(\frac{R_f}{R_3} \right) V_3 \right]$$

Thus the desired output:-

$$\frac{R_f}{R_1} = 3 \quad \text{or} \quad \frac{30k}{R_1} = 3 \quad \text{or} \quad R_1 = 10k\Omega$$

Similarly:-

$$\frac{R_f}{R_2} = 1 \quad \text{or} \quad R_f = R_2 = 30k\Omega$$

$$\text{and } \frac{R_f}{R_3} = 0.2 \Rightarrow R_3 = \frac{R_f}{0.2} \Rightarrow \frac{30k}{0.2k}$$

$$\Rightarrow R_3 = 150k$$

$$R = R_1 || R_2 || R_3 \Rightarrow 10k || 30k || 150k = 7k\Omega$$

Ans:- The gain in band pass region is that of non-inverting amplifier:-

$$A_v = \left(\frac{1+R_f}{R_1} \right) ; \quad A_v = 100 \quad R_1 = 1k$$
$$100 = \frac{1+R_f}{1k} \quad \text{or} \quad R_f = 99k\Omega$$

The cutoff frequency f_c for low-pass filter is given

by $f = \frac{1}{2\pi RC}$

$$\text{or } R = \frac{1}{2\pi f_c C} = \frac{1}{2 \times 3.14 \times 2 \times 10^3 \times 0.2 \times 10^{-6}}$$

$$= R = 398\Omega$$

Q.6

By definition CMRR

$$CMRR(dB) = 20 \log_{10} \left| \frac{A_v}{A_{cm}} \right|$$


$$A_d = 100 \text{ (given)} \Rightarrow A_{cm} = \frac{V_o}{V_{cm}} = \frac{0.01V}{1.0V} = 10^{-2}$$

therefore: - $CMRR = 20 \log_{10} \frac{100}{10^{-2}} \Rightarrow 20 \log_{10} (10^4)$

$$CMRR = 80dB$$


Q.3

Full wave Rectifier: -

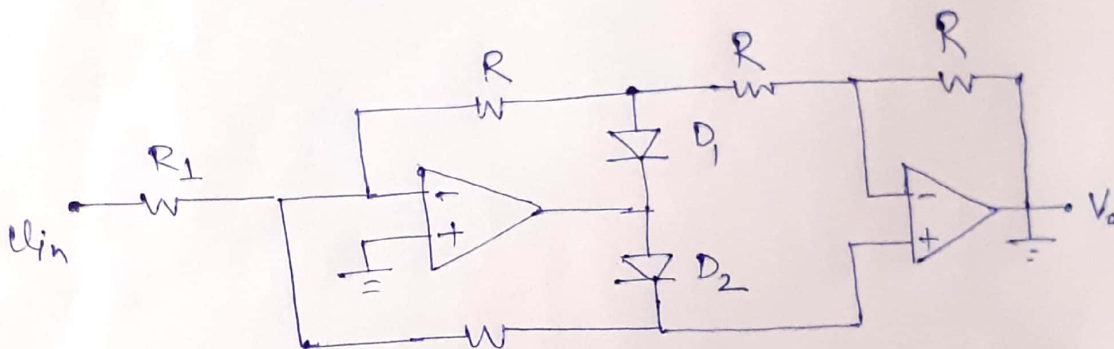

Assume: -

u_{in}

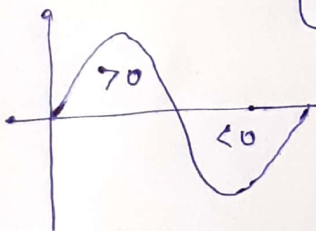

① $u_{in} > 0$:- D_1 - forward biased
 D_2 - Reverse biased.

$$V_o = \frac{-R}{R} \cdot \left(\frac{R}{R} \right) u_i \Rightarrow u_i$$

$$V_o = \frac{-2}{3} u_i$$

② $u_{in} < 0$ D_1 - Reverse biased
 D_2 - forward biased.

$$\frac{u_i}{R} + \frac{V}{2R} + \frac{V}{R} = 0$$

$$\frac{3V}{2R} = -\frac{u_i}{R}$$

$$V_o = \left(\frac{1+R}{2R} \right) V \Rightarrow \frac{3V}{2}$$

Substituting V in V_o

$$V_o = -\frac{3}{2} \left(\frac{-2}{3} V_i \right) = -V_i$$

