

Solution Mid-Sem Exam

①

Sub: Network Theory Branch: 6<sup>th</sup> Sem EC.

Sol<sup>n</sup> 1. (i)  $L f(s) = L(e^{-at} \cos \omega t) = \frac{s+a}{(s+a)^2 + \omega^2}$

(ii) In electrical or electronic ckt terminals are connecting point to connect with an external ckt. It is a point of entry or exit for electrical energy.

A port is a pair of terminals connecting an electrical network or ckt to an external circuit.

(iii)  $[Y] = [Z]^{-1} = \frac{1}{Z_{11}Z_{22} - Z_{12}Z_{21}} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix}$

$\Rightarrow Y_{22} = \frac{Z_{11}}{Z_{11}Z_{22} - Z_{12}Z_{21}} = \frac{0.9}{0.54 - 0.04}$

$Y_{22} = \frac{0.9}{0.5} = 1.8 \text{ mho. Ans.}$


(iv)  $Z_{11} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}}; Z_{12} = \frac{h_{12}}{h_{22}}$

$Z_{21} = \frac{-h_{21}}{h_{22}}; Z_{22} = \frac{1}{h_{22}}$

(v)

At  $t < 0^-$


Ckt is like

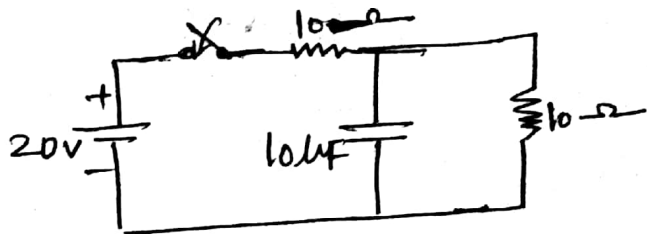

$$V_C(0^-) = 0.$$

At  $t(\infty)$  i.e. when steady state is reached

Ckt is like

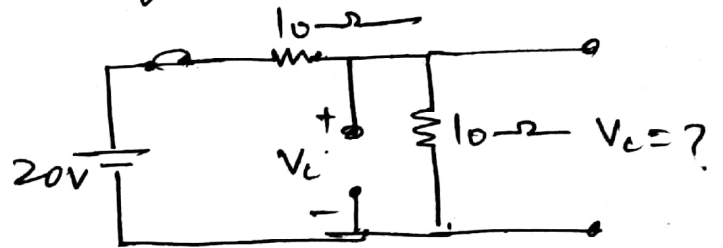


$$V_C(\infty) = 10 \text{ Volt.}$$


Ans: (2):

$$V_C(0^-) = 0.5 \text{ Volt.}$$

Given Ckt is like

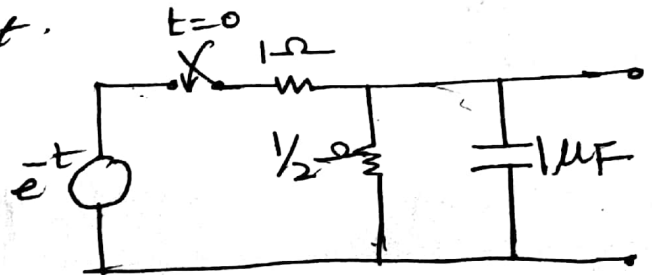

The Laplace equivalent Ckt will be given

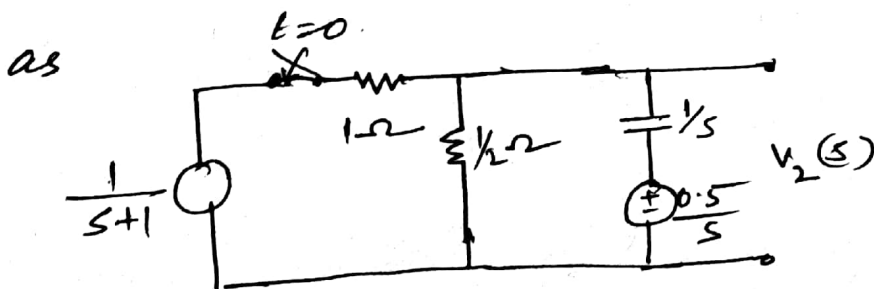

Applying KCL

$$\frac{1}{s+1} - V_2(s) = \frac{V_2(s)}{1/2} + \frac{V_2(s) - \frac{0.5}{s}}{1/s}$$

or

$$\frac{1}{s+1} + 0.5 = (3+s) V_2(s)$$

$$\Rightarrow V_2(s) = \frac{1 + 0.5(s+1)}{(s+3)(s+1)} = \frac{0.5(s+3)}{(s+3)(s+1)}$$

$$V_2(s) = \frac{0.5}{s+1}$$

Taking inverse Laplace


We get:  $V_2(t) = 0.5 \cdot e^{-t} \text{ Volt}$  Ans

Ans: (3) At time  $t < 0$ , ckt is in steady state cond<sup>n</sup>.

At  $t < 0^+$

$$I_L(0^-) = \frac{10}{2} = 5 \text{ Amp.}$$


$$I_L(0^+) = I_L(0^-) = 5 \text{ Amp}$$

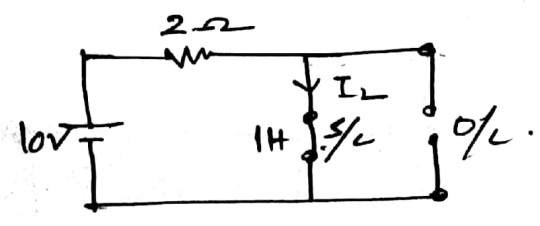

At  $t > 0^+$ ; ckt will be like as below:

Applying KVL in the ckt.
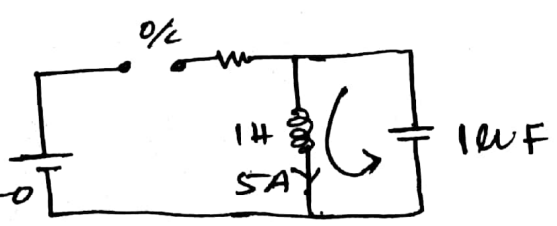
$$L \frac{di_L(t)}{dt} + \frac{1}{C} \int i_L(t) dt = 0$$



Taking Laplace transform, we have:

$$L [s I_L(s) - i_L(0^+)] + \frac{1}{C} \frac{I_L(s)}{s} = 0$$

$$(L \cdot s + \frac{1}{Cs}) I_L(s) = L \cdot \frac{V}{R}$$


$$I_L(s) = \frac{LV}{R} \frac{Cs}{Lcs^2 + 1} = \frac{V}{R} \frac{s}{s^2 + \frac{1}{LC}} \quad \text{--- (1)}$$

Taking inverse Laplace of eqn ①

We get  $i_L(t) = \frac{V}{R} \cdot \cos \frac{1}{\sqrt{LC}} t$

$\Rightarrow i_L(t) = 5 \cdot \cos 10^3 t$  Amp Ans.

Ans: (4)

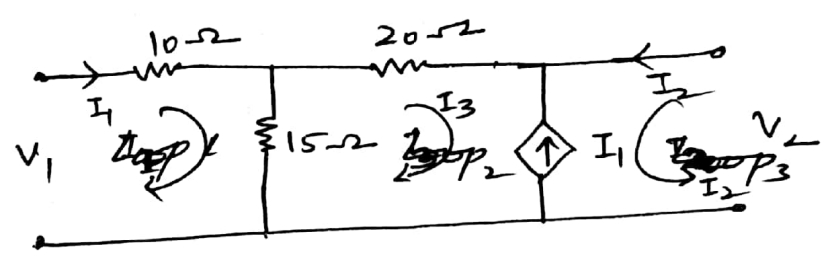

Applying KVL in loop 1.

We get:

$-V_1 + 10I_1 + 15(I_1 + I_2) = 0$

$\Rightarrow V_1 = 10I_1 + 30I_1 + 15I_2$

$\Rightarrow V_1 = 40I_1 + 15I_2$  — ①

Again applying KVL in loop 2 & loop 3

We get

$-V_2 + 20(I_1 + I_2) + 15(2I_1 + I_2) = 0$

$\Rightarrow V_2 = 20I_1 + 20I_2 + 30I_1 + 15I_2$

$\Rightarrow V_2 = 50I_1 + 35I_2$  — ②


(5)

Equating eqn ① & eqn ② with  
standard Z-parameters

We get:

$$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 40 & 15 \\ 50 & 35 \end{bmatrix}$$

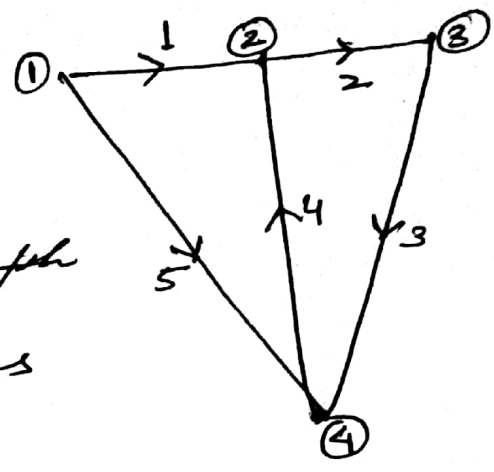Ans: (5) The given graph is as shown figure.



The incidence matrices of the graph may be shown as below.

No. of nodes = 4

No. of branches = 5

Nodes	Branches				
	1	2	3	4	5
1	1	0	0	0	1
2	-1	1	0	-1	1
3	0	-1	1	0	0
4	0	0	-1	1	-1