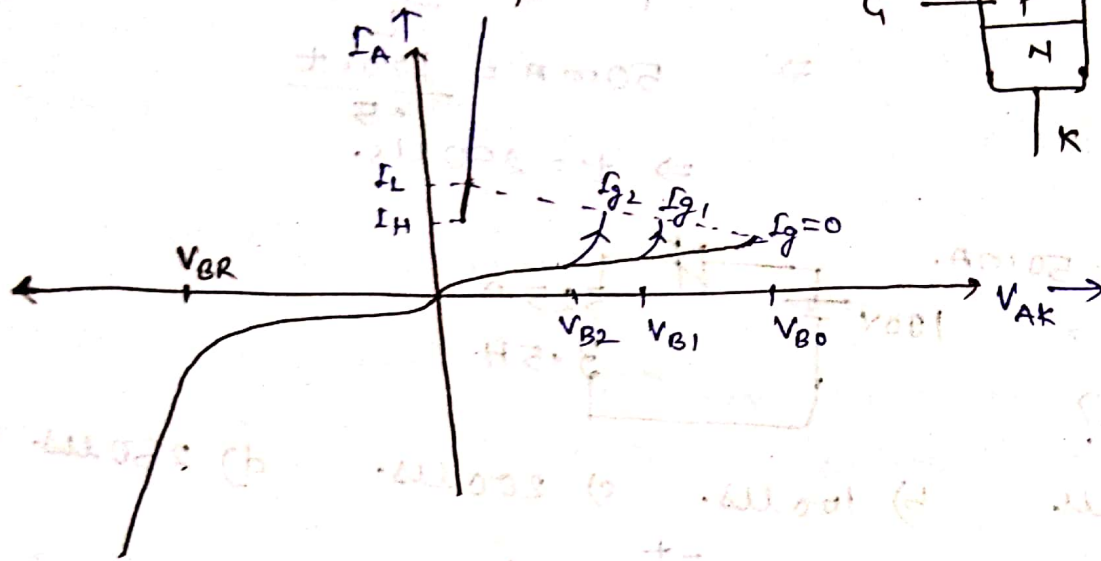


I-V. Characteristic of SCR:-




Significance of Latching current:-

- Latching current is related to the turn on process.
- Gate signal initiates the turn on process, but once the SCR is in on state gate loses control over the device. Hence therefore we remove the gate sig when SCR becomes on to avoid the cont. gate power loss.
- If we remove the gate signal when anode current is lesser than the latching value then SCR fails to turn on. Therefore we must maintain the gate pulse width atleast for a period until gate current reaches certain min^m. value.
- Latching current is specified to estimate the min^m. gate pulse width requirement to turn on the SCR.

Q(2) $I_L = 50 \text{ mA}$.

$t_{on} = ?$

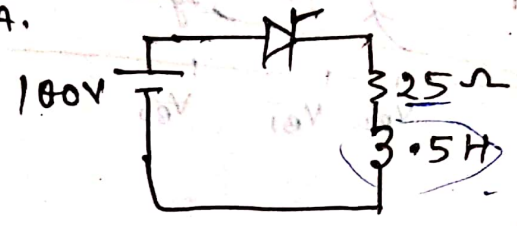

- a) 250 μs. b) 100 μs. c) 200 μs. d) 250 μs.

Sol.

$$i_L(t) = (i_0^+ - i_0^-) e^{-\frac{t}{\tau}} + i_0^-$$

$$= (0 - 4) e^{-\frac{t \cdot R}{L}} + 4$$

$$= 4 \left(1 - e^{-\frac{t \cdot 25}{3.5}} \right)$$

$$50 \times 10^{-3} = 4 \left(50 \text{ mA} - 4 \right) = -4 e^{-\frac{tR}{L}}$$

$$\Rightarrow e^{-\frac{25t}{3.5}} = \frac{1}{4} (4 - 0.05)$$

$$e^{-50t} = \frac{1}{4} (3.95)$$

$$-50t = -0.0125$$

$$t = 250 \mu\text{s}$$

Q. The i/p voltage given to 1- ϕ full wave conv. is

② $V_1 = 100\sqrt{2} \sin(100\pi t)$. The i drawn by conv. is

$$i = 10\sqrt{2} \sin(100\pi t - \pi/3) + 5\sqrt{2} \sin(300\pi t + \pi/4) + 2\sqrt{2} \sin(500\pi t - \pi/6)$$

① The i/p pf of converter.

② The active power drawn by converter.

Soln. - ① $\therefore \text{CDF} = \frac{I_{s1}}{I_{sr}} \therefore \text{P.P.F} = \text{CDF} \cdot \text{D.F.}$

$$I_{s1} = \frac{10\sqrt{2}}{\sqrt{2}} = 10 \text{ A.}, \quad I_{sr} = \sqrt{10^2 + 5^2 + 2^2}$$

$$= \sqrt{129}$$

$$= 11.36 \text{ A}$$

$$\therefore \text{CDF} = \frac{10}{11.36}$$

$$\text{D.F} = \cos \pi/3 = 0.5$$

$$\therefore \text{P.P.F} = \frac{10}{11.36} \times 0.5 = 0.440.$$

② Active power delivered to load,





$$P = V_{sr} \cdot I_{sr} \cdot \cos \phi$$

$$= 100 \times 10 \times \frac{1}{2} = 500 \text{ W.}$$

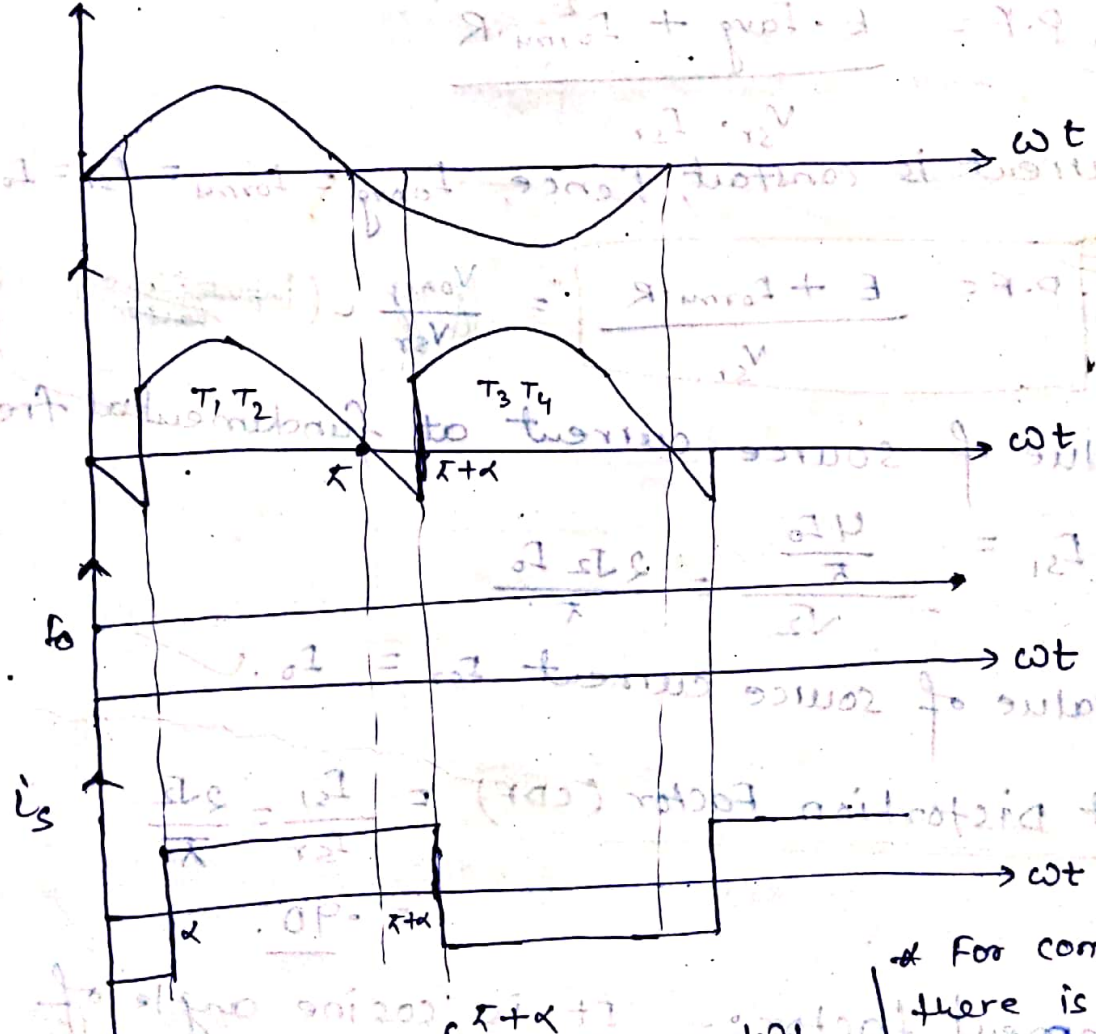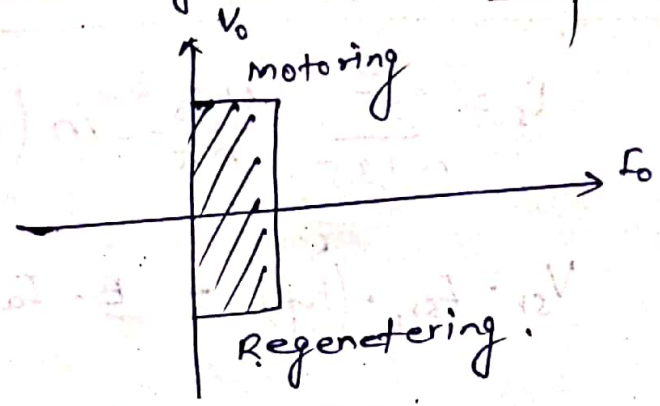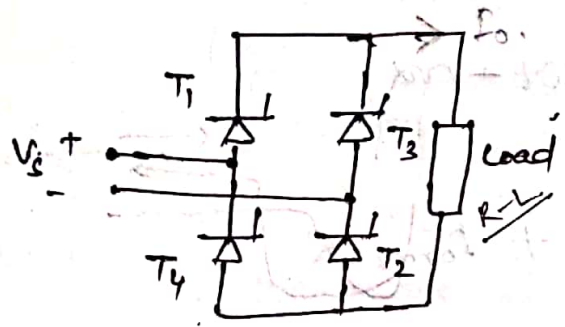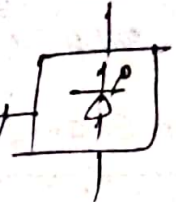3) 1- ϕ Full Wave bridge converter:-

→ It is used for two quadrant operation.

→ used for motoring and regenerating operation.



$$V_{oAvg} = \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t$$

$$V_{oAvg} = \frac{2 V_m \cos \alpha}{\pi}$$

* For R-L-E load-

$$V_{oAvg} = I_{oAvg} R + E$$

$$\therefore I_{oAvg} = \frac{V_{oAvg} - E}{R}$$

* For continuous conduction there is no effect of back emf in the o/p voltage.

* The cont. cond? wave form will remain same for R-L and R-L-E load.


$$V_{oAvg} = \frac{2 V_m \cos \alpha}{\pi}$$

for both RL & RLE load.


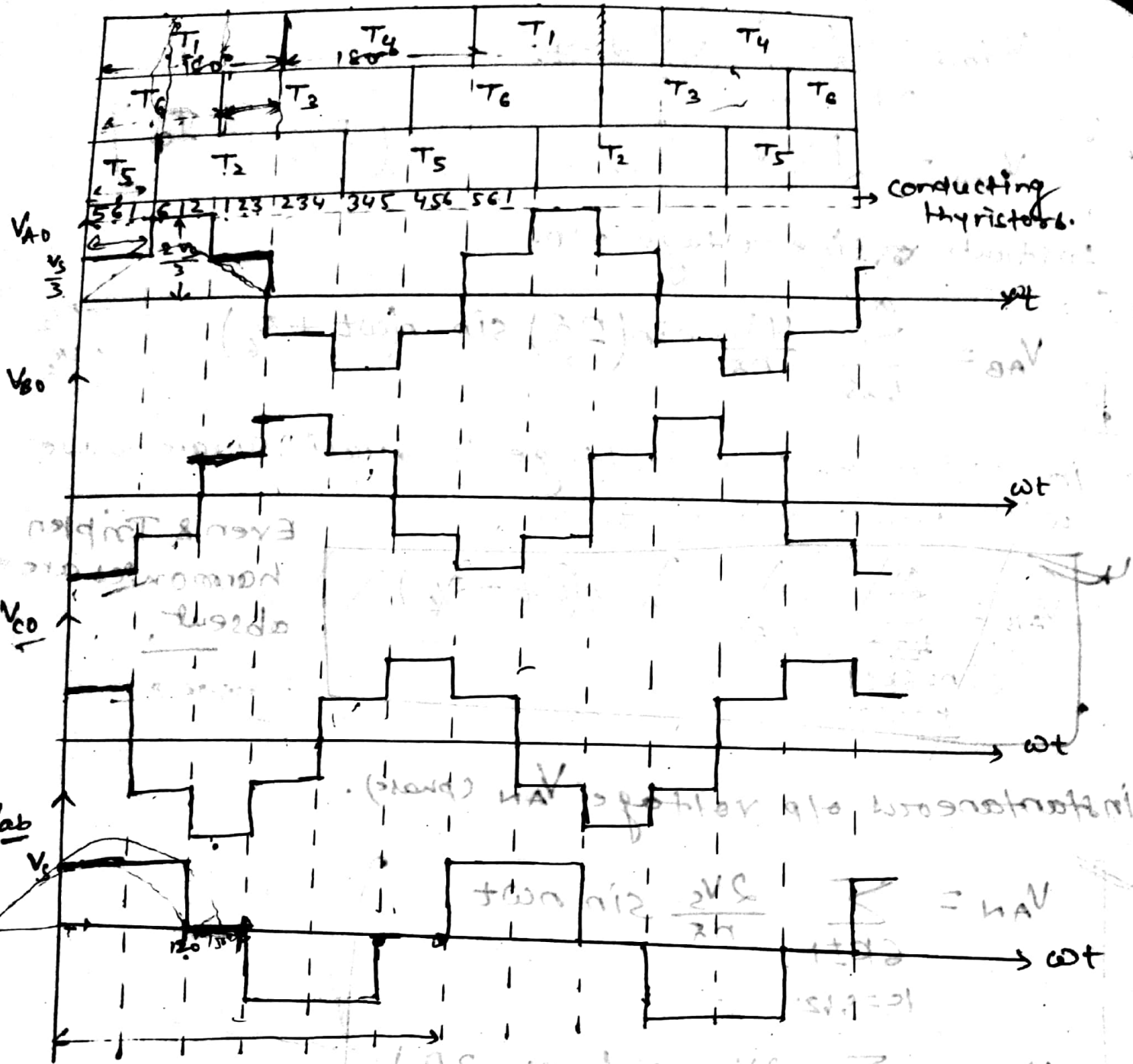
(3) (ii) 180° (180, 60)

180° conduction mode:-

- * Each T conducts for 180°
- * The phase angle between one switching devices other is 60°
- * At any instant of time 3-switching devices are conducting.
- * The phase voltage wave form is 3-stepped sq. wave.
- * The line voltage is quasi sq. wave.
- * Commutation time for the same leg switching devices is zero. ⇒ Drawback.



0-60° → T_1, T_5, T_6 → ON.

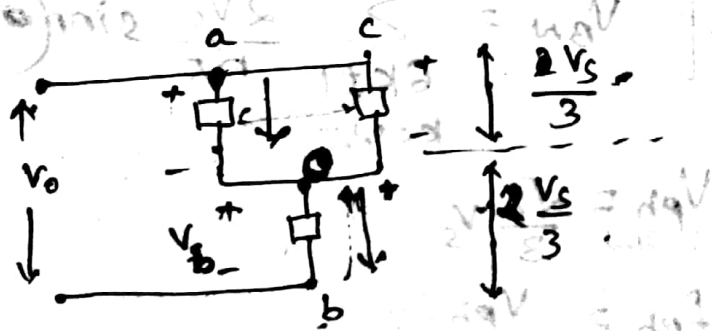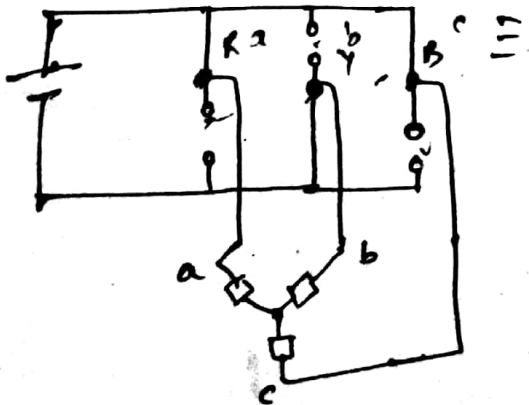

$$V_{a0} = V_{c0} = \frac{V_s}{3}$$

$$V_{b0} = -\frac{2V_s}{3}$$

$$V_{Lrms} = \sqrt{\frac{1}{\pi} \int_0^{2\pi/3} (V_s)^2 d\omega t}$$

$$V_{Lrms} = \sqrt{\frac{2}{3}} V_s$$

$$I_{sr} = \sqrt{\frac{2}{3}} I_o$$

Instantaneous line voltage of P.

$$V_{AB} = \sum_{1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin\left(\frac{n\pi}{3}\right) \sin n(\omega t + \pi/6)$$

$-\pi/2$
 $+\pi/6$



(iii) Pulse Width Modulation Technique:-

- Instead of applying gate pulse $T/2$ or 180° period, vary the pulse width 0 to $T/2$ or 0 to 180° , so that the o/p voltage is controllable.
- We can control the voltage within the inverter itself without increasing the no. of stages.
- We can also eliminate some of the lower harmonics.
- We can easily filter higher order harmonics using small size filter.

Types-

(1) Single pulse modulation Technique:-

For 1- ϕ Full bridge inverter:-

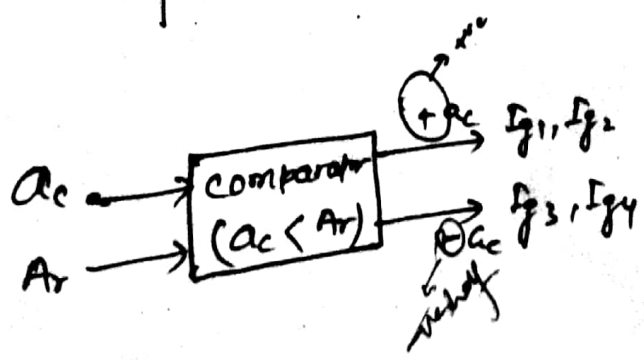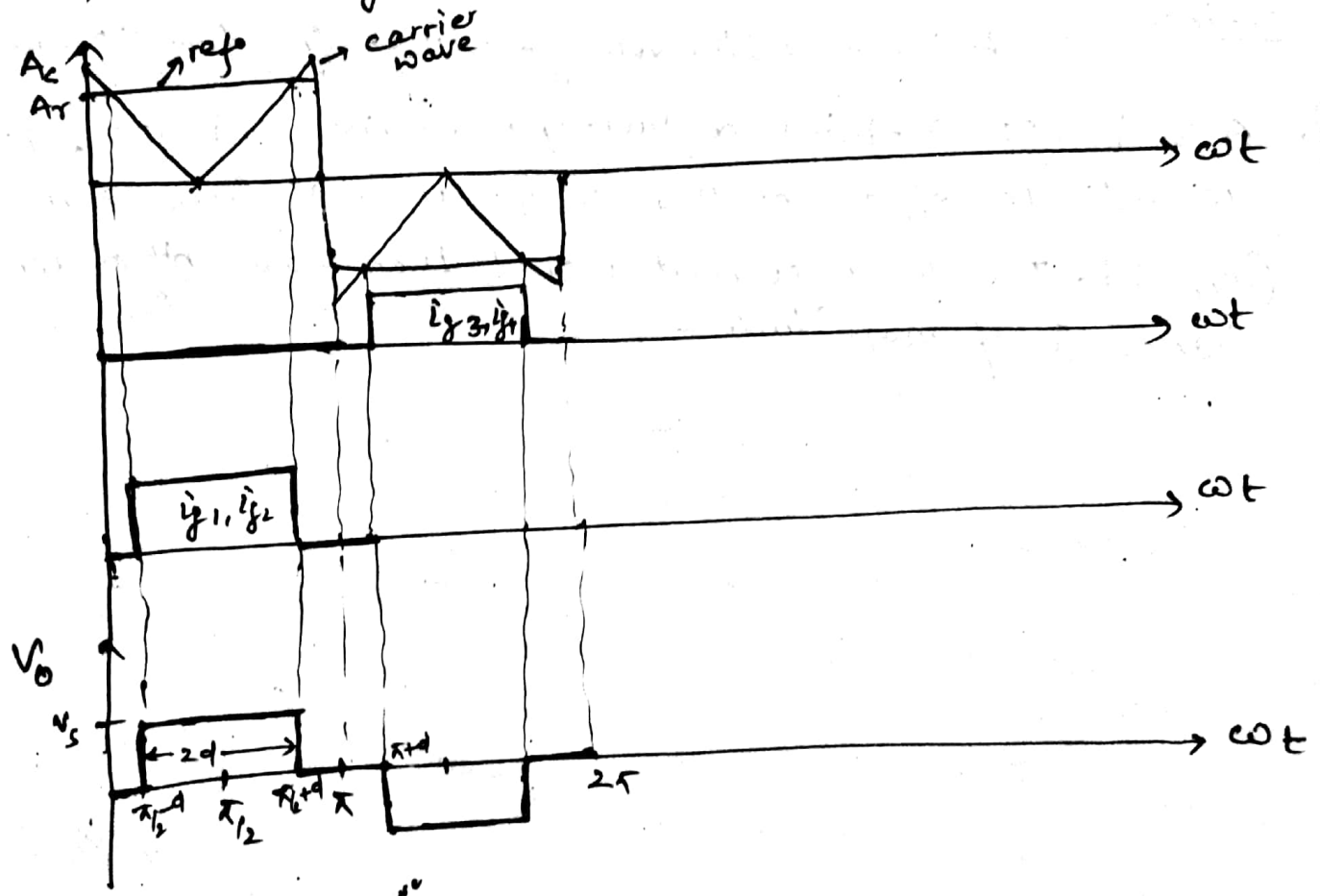

O/P RMS voltage,

$$V_{\text{orms}} = \sqrt{\frac{1}{\pi} \int_{\pi/2-d}^{\pi/2+d} V_s^2 \cdot d\omega t}$$

$$V_{\text{orms}} = V_s \cdot \sqrt{\frac{2d}{\pi}} \Rightarrow V_{\text{orms}} = V_s \cdot \sqrt{\frac{\text{pulse width}}{\pi}}$$

HARMONIC ANALYSIS:-

$$V_o = \sum_{n=1,3,5}^{\infty} \frac{4V_s}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cdot \sin(nd) \cdot \sin(n\omega t)$$

$$V_{on} = \frac{4V_s}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cdot \sin(nd) \cdot \sin(n\omega t)$$

→ +L (+ve volt)
→ -L (-ve volt)
→ 0 for n=even

To eliminate n^{th} harmonic,

$$V_{on} = 0 \Rightarrow \sin nd = 0$$

$$nd = \pi$$

$$d = \frac{\pi}{n}$$

pulse width.

$$2d = \frac{2\pi}{n}$$

Ex. To eliminate 3rd harmonic,

$$\sin 3d = 0$$

$$3d = \pi$$

$$d = \frac{\pi}{3}$$

$$2d = \frac{2\pi}{3}$$

72° pulse width for elimination of 3rd harm.